

IC設計實驗期中考練習1 2024

班級:_____ 學號:_____ 姓名:_____ 成績:_____

1. The input signal rising/falling time is 0.5ns. The output loading is 1pf. Please design the 3-input dynamic XOR with the same delay time as 1ns for various input patterns. ($0.95\text{ns} < T_{000}, T_{001}, T_{010}, T_{011}, T_{100}, T_{101}, T_{110}, T_{111} < 1.05\text{ns}$) **(Function Validation: 30%, $0.8\text{ns} < \text{Delay} < 1.2\text{ns}$: 30%, $0.9\text{ns} < \text{Delay} < 1.1\text{ns}$: 10%, $0.95\text{ns} < \text{Delay} < 1.05\text{ns}$: 10%)**
2. Please write down your consideration during constructing function and sizing procedure. **(20%)**

IC設計實驗期中考練習2 2024

班級:_____ 學號:_____ 姓名:_____ 成績:_____

1. The input signal rising/falling time is 0.5ns. The output loading is 1pf. Please design the 3-input pseudo nMOS XOR with the same delay time as 1ns for various input patterns. ($0.95\text{ns} < T_{000}, T_{001}, T_{010}, T_{011}, T_{100}, T_{101}, T_{110}, T_{111} < 1.05\text{ns}$) **(Function Validation: 30%, 0.8ns < Delay < 1.2ns: 30%, 0.9ns < Delay < 1.1ns: 10%, 0.95ns < Delay < 1.05ns: 10%)**
2. Please write down your consideration during constructing function and sizing procedure. **(20%)**

IC設計實驗期中考練習3 2024

班級:_____ 學號:_____ 姓名:_____ 成績:_____


1. The input signal rising/falling time is 0.5ns. The output loading is 1pf. Please design the 3-input pass-transistor XOR with the same delay time as 1ns for various input patterns. ($0.95\text{ns} < T_{000}, T_{001}, T_{010}, T_{011}, T_{100}, T_{101}, T_{110}, T_{111} < 1.05\text{ns}$) **(Function Validation: 30%, 0.8ns < Delay < 1.2ns: 30%, 0.9ns < Delay < 1.1ns: 10%, 0.95ns < Delay < 1.05ns: 10%)**
2. Please write down your consideration during constructing function and sizing procedure. **(20%)**

IC設計實驗期中考練習4 2024

班級:_____ 學號:_____ 姓名:_____ 成績:_____

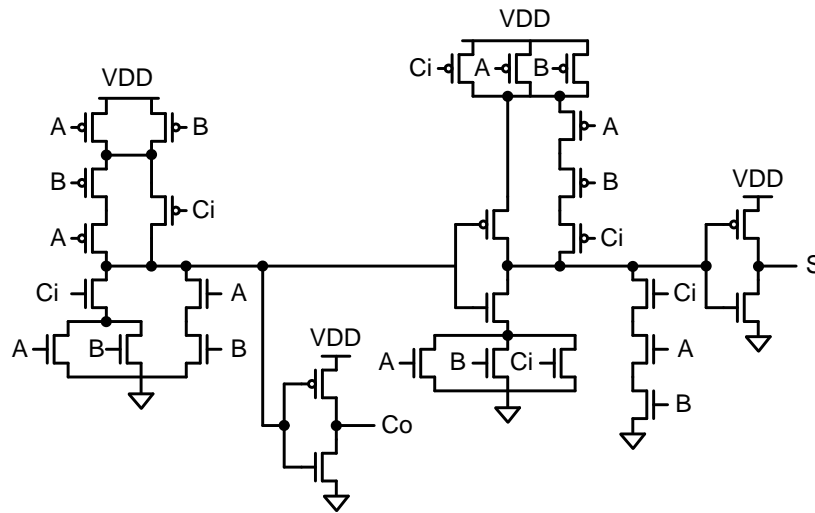1. The input signal rising/falling time is 0.5ns. The output loading of Co and S is 1pf. Please design the single bit pseudo-nMOS Full-adder with the same rising time and falling time as 1ns in both S and Co. ($0.95\text{ns} < T_{000}, T_{001}, T_{010}, T_{011}, T_{100}, T_{101}, T_{110}, T_{111} < 1.05\text{ns}$) (You can only tune the size of transistor. Altering the circuit architecture is not allowed.)

(Function Validation: 30%, $0.8\text{ns} < \text{Delay} < 1.2\text{ns}$: 30%, $0.9\text{ns} < \text{Delay} < 1.1\text{ns}$: 10%, $0.95\text{ns} < \text{Delay} < 1.05\text{ns}$: 10%)



(Reference Full-Adder Circuit)


2. Please write down your consideration during constructing function and sizing procedure. (20%)

IC設計實驗期中考練習5 2024

班級:_____ 學號:_____ 姓名:_____ 成績:_____

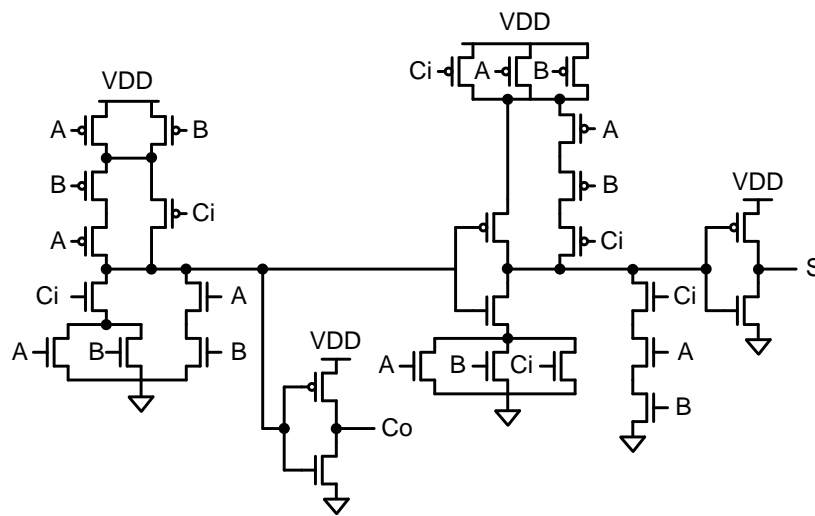1. The input signal rising/falling time is 0.5ns. The output loading of Co and S is 1pf. Please design the single bit dynamic CMOS Full-adder with the same rising time and falling time as 1ns in both S and Co. ($0.95\text{ns} < T_{000}, T_{001}, T_{010}, T_{011}, T_{100}, T_{101}, T_{110}, T_{111} < 1.05\text{ns}$) (You can only tune the size of transistor. Altering the circuit architecture is not allowed.)

(Function Validation: 30%, $0.8\text{ns} < \text{Delay} < 1.2\text{ns}$: 30%, $0.9\text{ns} < \text{Delay} < 1.1\text{ns}$: 10%, $0.95\text{ns} < \text{Delay} < 1.05\text{ns}$: 10%)



(Reference Full-Adder Circuit)

2. Please write down your consideration during constructing function and sizing procedure. (20%)

IC設計實驗期中考練習6 2024

班級:_____ 學號:_____ 姓名:_____ 成績:_____

1. The input signal rising/falling time is 0.5ns. The output loading is 0.5pf. Please design the 3-input pass-transistor $A*B+C*(B*D+A*E)$ with the same delay time as 1ns for various input patterns. ($0.95\text{ns} < T_{000}, T_{001}, T_{010}, T_{011}, T_{100}, T_{101}, T_{110}, T_{111} < 1.05\text{ns}$) **(Function Validation: 30%, 0.8ns < Delay < 1.2ns: 30%, 0.9ns < Delay < 1.1ns: 10%, 0.95ns < Delay < 1.05ns: 10%)**
2. Please write down your consideration during constructing function and sizing procedure. **(20%)**

IC設計實驗期中考練習7 2024

班級:_____ 學號:_____ 姓名:_____ 成績:_____

1. The input signal rising/falling time is 0.5ns. The output loading of $A=B$, $A>B$, and $A<B$ are all 0.5pf. Please design the comparator by using pseudo-nMOS with the same rising time and falling time as 1ns. ($0.95\text{ns} < T_{00}, T_{01}, T_{10}, T_{11} < 1.05\text{ns}$) (You can only tune the size of transistor. Altering the circuit architecture is not allowed.)

(Function Validation: 30%, $0.8\text{ns} < \text{Delay} < 1.2\text{ns}$: 30%, $0.9\text{ns} < \text{Delay} < 1.1\text{ns}$: 10%, $0.95\text{ns} < \text{Delay} < 1.05\text{ns}$: 10%)

表 1 一位元數位比較器真值表

輸入		輸出		
a	b	$a < b$	$a = b$	$a > b$
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

 


圖 1 一位元數位比較器電路圖

2. Please write down your consideration during constructing function and sizing procedure. (20%)

IC設計實驗期中考練習8 2024

班級:_____ 學號:_____ 姓名:_____ 成績:_____

- The input signal rising/falling time is 0.5ns. The output loading of $A=B$, $A>B$, and $A<B$ are all 0.5pf. Please design the comparator by using dynamic CMOS logic with the same rising time and falling time as 1ns. ($0.95\text{ns} < T_{00}, T_{01}, T_{10}, T_{11} < 1.05\text{ns}$) (You can only tune the size of transistor. Altering the circuit architecture is not allowed.)

(Function Validation: 30%, $0.8\text{ns} < \text{Delay} < 1.2\text{ns}$: 30%, $0.9\text{ns} < \text{Delay} < 1.1\text{ns}$: 10%, $0.95\text{ns} < \text{Delay} < 1.05\text{ns}$: 10%)

表 1 一位元數位比較器真值表

輸入		輸出		
a	b	$a < b$	$a = b$	$a > b$
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

 


圖 1 一位元數位比較器電路圖

- Please write down your consideration during constructing function and sizing procedure. (20%)

IC設計實驗期中考練習9 2024

班級:_____ 學號:_____ 姓名:_____ 成績:_____

1. The input signal rising/falling time is 0.5ns. The output loading of A=B, A>B, and A<B are all 2pf. Please design the comparator by using pass-transistor with the same rising time and falling time as 1ns. ($0.95\text{ns} < T_{00}, T_{01}, T_{10}, T_{11} < 1.05\text{ns}$) (You can only tune the size of transistor. Altering the circuit architecture is not allowed.)

(Function Validation: 30%, $0.8\text{ns} < \text{Delay} < 1.2\text{ns}$: 30%, $0.9\text{ns} < \text{Delay} < 1.1\text{ns}$: 10%, $0.95\text{ns} < \text{Delay} < 1.05\text{ns}$: 10%)

表 1 一位元數位比較器真值表

輸入		輸出		
a	b	$a < b$	$a = b$	$a > b$
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

 


圖 1 一位元數位比較器電路圖

2. Please write down your consideration during constructing function and sizing procedure. (20%)

IC設計實驗期中考練習10 2024

班級:_____ 學號:_____ 姓名:_____ 成績:_____

3. The input signal rising/falling time is 0.5ns. The output loading is 2pf. Please design the circuit by using pass-transistor with the same rising time and falling time as 1ns. ($0.95\text{ns} < T_{00}, T_{01}, T_{10}, T_{11} < 1.05\text{ns}$)

(Function Validation: 30%, $0.8\text{ns} < \text{Delay} < 1.2\text{ns}$: 30%, $0.9\text{ns} < \text{Delay} < 1.1\text{ns}$: 10%, $0.95\text{ns} < \text{Delay} < 1.05\text{ns}$: 10%)

 


圖1 要求相關電路

4. Please write down your consideration during constructing function and sizing procedure.
(20%)