

# IC設計實驗期中考

班級:\_\_\_\_\_ 學號:\_\_\_\_\_ 姓名:\_\_\_\_\_ 成績:

The input signal rising/falling time is 0.5ns. The output loading is 0.5pf. Please design the **3-input dynamic XOR** with **the same delay time as 0.5ns** for various input patterns. ( $0.4\text{ns} < T_{000}, T_{001}, T_{010}, T_{011}, T_{100}, T_{101}, T_{110}, T_{111} < 0.6\text{ns}$ ) **(Function Validation: 50%,  $0.3\text{ns} < \text{Delay} < 0.7\text{ns}$ : 30%,  $0.4\text{ns} < \text{Delay} < 0.6\text{ns}$ : 20%)**

## IC設計實驗期中考

班級:\_\_\_\_\_ 學號:\_\_\_\_\_ 姓名:\_\_\_\_\_ 成績:

The input signal rising/falling time is 0.2ns. The output loading is 0.5pf. Please design the **3-input pseudo nMOS XOR** with the same delay time as 1ns for various input patterns. ( $0.4\text{ns} < T_{000}, T_{001}, T_{010}, T_{011}, T_{100}, T_{101}, T_{110}, T_{111} < 0.6\text{ns}$ ) (**Function Validation: 50%,  $0.3\text{ns} < \text{Delay} < 0.7\text{ns}$ : 30%,  $0.4\text{ns} < \text{Delay} < 0.6\text{ns}$ : 20%**)

## IC設計實驗期中考

班級:\_\_\_\_\_ 學號:\_\_\_\_\_ 姓名:\_\_\_\_\_ 成績:

The input signal rising/falling time is 0.2ns. The output loading is 0.5pf. Please design the **3-input pass-transistor XOR** with the same delay time as 0.5ns for various input patterns. ( $0.4\text{ns} < T_{000}, T_{001}, T_{010}, T_{011}, T_{100}, T_{101}, T_{110}, T_{111} < 0.6\text{ns}$ ) (**Function Validation: 50%,  $0.3\text{ns} < \text{Delay} < 0.7\text{ns}$ : 30%,  $0.4\text{ns} < \text{Delay} < 0.6\text{ns}$ : 20%**)




## IC設計實驗期中考

班級:\_\_\_\_\_ 學號:\_\_\_\_\_ 姓名:\_\_\_\_\_ 成績:

The input signal rising/falling time is 0.5ns. The output loading of Co and S is 0.5pf. Please design the **single bit pseudo-nMOS Full-adder** with the same rising time and falling time as 0.6ns in both S and Co. ( $0.5\text{ns} < T_{000}, T_{001}, T_{010}, T_{011}, T_{100}, T_{101}, T_{110}, T_{111} < 0.7\text{ns}$ ) (You can only tune the size of transistor. Altering the circuit architecture is not allowed.)

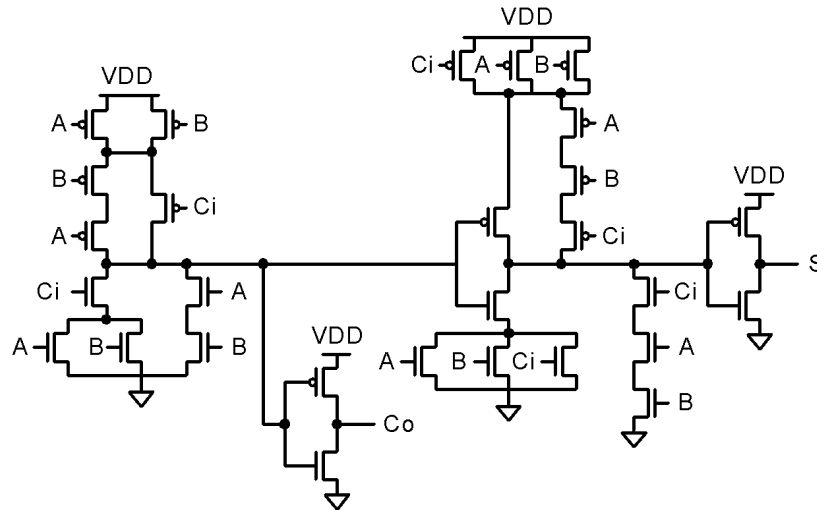**(Function Validation: 50%,  $0.4\text{ns} < \text{Delay} < 0.8\text{ns}$ : 30%,  $0.5\text{ns} < \text{Delay} < 0.7\text{ns}$ : 20%)**




(Reference Full-Adder Circuit)

## IC設計實驗期中考

班級:\_\_\_\_\_ 學號:\_\_\_\_\_ 姓名:\_\_\_\_\_ 成績:

The input signal rising/falling time is 0.5ns. The output loading of Co and S is 1pf. Please design the **single bit dynamic CMOS Full-adder** with the same rising time and falling time as 1ns in both S and Co. ( $0.9\text{ns} < T_{000}, T_{001}, T_{010}, T_{011}, T_{100}, T_{101}, T_{110}, T_{111} < 1.1\text{ns}$ ) (You can only tune the size of transistor. Altering the circuit architecture is not allowed.)

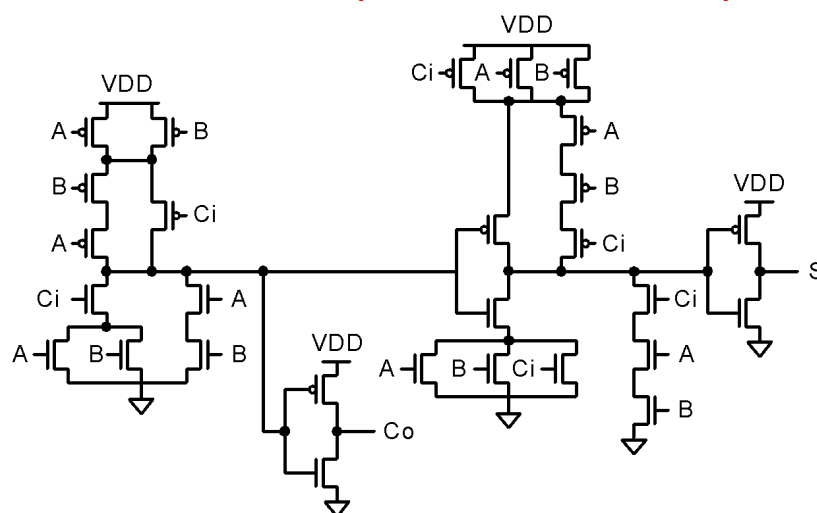(Function Validation: 50%, 0.8ns < Delay < 1.2ns: 30%, 0.9ns < Delay < 1.1ns: 20%)



(Reference Full-Adder Circuit)

# IC設計實驗期中考

班級:\_\_\_\_\_學號:\_\_\_\_\_姓名:\_\_\_\_\_成績:\_\_\_\_\_

The input signal rising/falling time is 0.5ns. The output loading of A=B, A>B, and A<B are all 0.5pf. Please design the comparator by using **pseudo-nMOS** with the same rising time and falling time as 0.5ns. ( $0.4\text{ns} < T_{00}, T_{01}, T_{10}, T_{11} < 0.6\text{ns}$ ) (You can only tune the size of transistor. Altering the circuit architecture is not allowed.)

(Function Validation: 50%, 0.3ns < Delay < 0.7ns: 30%, 0.4ns < Delay < 0.6ns: 20%)

表 1 一位元數位比較器真值表

輸入		輸出		
a	b	$a < b$	$a = b$	$a > b$
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

 


圖 1 一位元數位比較器電路圖

# IC設計實驗期中考

班級: 學號: 姓名: 成績:

The input signal rising/falling time is 0.5ns. The output loading of A=B, A>B, and A<B are all 0.5pf. Please design **the comparator by using dynamic CMOS logic** with the same rising time and falling time as 0.5ns. ( $0.4\text{ns} < T_{00}, T_{01}, T_{10}, T_{11} < 0.6\text{ns}$ ) (You can only tune the size of transistor. Altering the circuit architecture is not allowed.)

(Function Validation: 50%,  $0.3\text{ns} < \text{Delay} < 0.7\text{ns}$ : 30%,  $0.4\text{ns} < \text{Delay} < 0.6\text{ns}$ : 20%)

表 1 一位元數位比較器真值表

輸入		輸出		
a	b	$a < b$	$a = b$	$a > b$
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

 


圖 1 一位元數位比較器電路圖

## IC設計實驗期中考

班級:\_\_\_\_\_ 學號:\_\_\_\_\_ 姓名:\_\_\_\_\_ 成績:

The input signal rising/falling time is 0.5ns. The output loading of  $A=B$ ,  $A>B$ , and  $A<B$  are all 0.5pf. Please design the comparator by using **pass-transistor** with the same rising time and falling time as 0.6ns. ( $0.5\text{ns} < T_{00}, T_{01}, T_{10}, T_{11} < 0.7\text{ns}$ ) (You can only tune the size of transistor. Altering the circuit architecture is not allowed.)

**(Function Validation: 50%,  $0.4\text{ns} < \text{Delay} < 0.8\text{ns}$ : 30%,  $0.5\text{ns} < \text{Delay} < 0.7\text{ns}$ : 20%)**

表 1 一位元數位比較器真值表

輸入		輸出		
a	b	$a < b$	$a = b$	$a > b$
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

 


圖 1 一位元數位比較器電路圖